

# *Combined Analog/Digital Spectral Testing for RF and DSP Circuits for Wireless Applications*

Abhishek Bisaria

Michael L. Bushnell

CAIP Center and WINLAB

ECE Dept., Rutgers U., Piscataway, NJ

## ***Funding Agencies***

***New Jersey Commission on Science and Technology***

***National Science Foundation***


# *Overall Research Effort*

- Fall 2001 research projects completed:
  - *Vivek Gaur – Redundancy identification with implication graphs*
  - *Aditya Sathe -- New analog coupling fault model for digital circuit faults due to capacitive, resistive, and inductive coupling in interconnect*
  - *Lan Rao -- New IDDQ current testing signatures to cut the yield loss of IDDQ testing*
  - *Tezaswi Raja – Transistor resizing for minimizing power consumption (due to glitches) while speeding up the circuit*
- Related external grants:
  - **NSF -- CCR-9988239 \$131,776 Low-Power SoC Design for Minimum Transient Energy**
  - **NSF -- CCR-0098304 \$513,523 Spectral Analysis for Mixed-Signal SoC Testing and Verification**

# *Outline*

- Introduction
- Background
  - *Boundary scan and Analog Test Bus*
  - *DSP-based Testing of Mixed-Signal Circuits*
  - *Prior Work*
- Proposed Combined Digital / Analog Test Method
- Test frequency generation for analog module
  - *With combinational digital circuits*
  - *With sequential digital circuits*
- Digital module testing in analog frequency domain
- Conclusions and Future work

# *Example System-on-a-Chip*

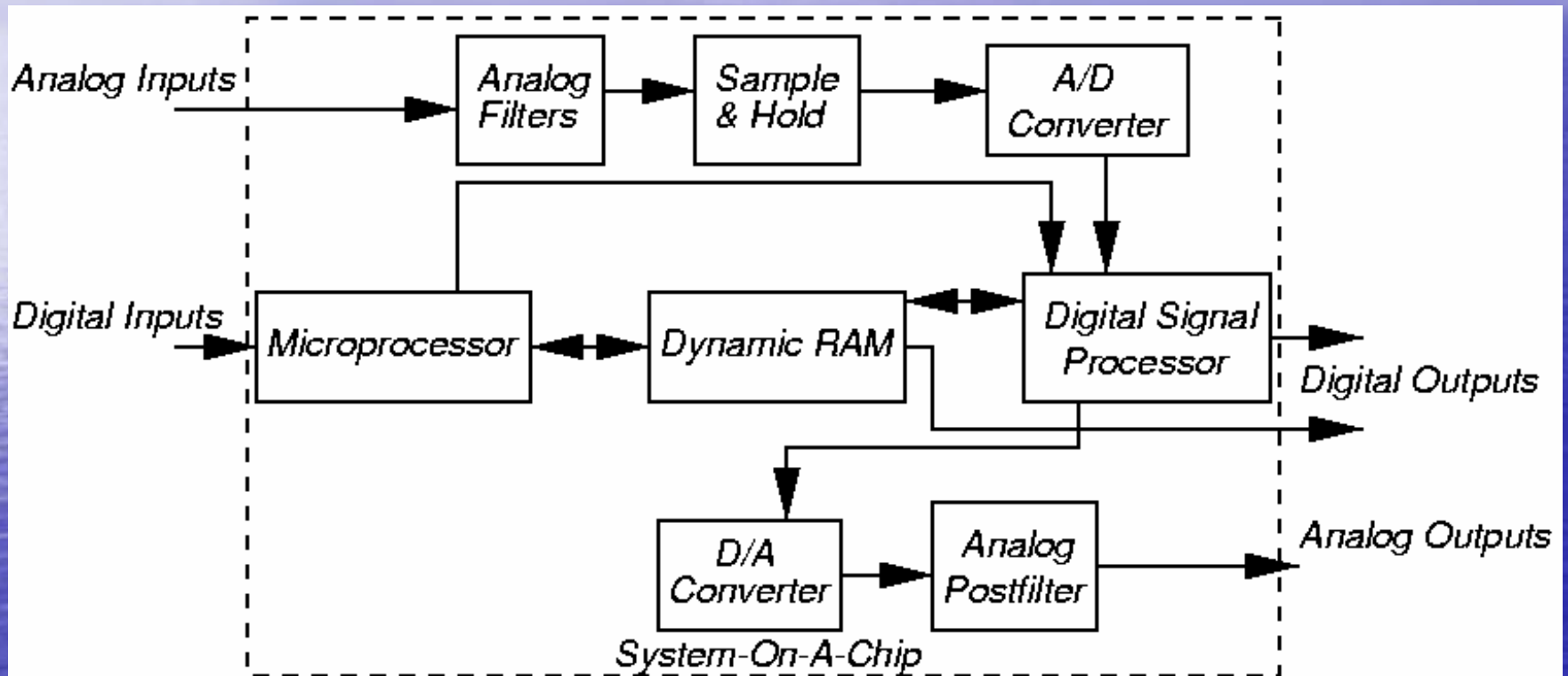


# *Introduction*

- System-on-a-chip (SoC)
  - *A single chip replaces the whole PCB (Printed Circuit Board)*
  - *Different chips on the PCB are now the building blocks of a SoC chip.*
  - *Advantages:*
    - On-chip interconnects are many times faster than off-chip wires
    - Get a compact system with the same functionality
    - Reduces pin overhead
      - *Saves a lot of power*
      - *Reduces noise in the mixed-signal/analog circuits*
  - *Liabilities*
    - Bed-of-nails testing of the system is not possible
    - Most of the blocks are surrounded by many other blocks
      - *Results in very poor controllability and observability*
      - *Need for test hardware to access these blocks during the testing*

# *Present Testing Method*

- Build hardware *test busses* between all memories, digital circuits, and analog circuits
- Use *built-in self-test* to test memories
- Testing procedure:
  - *Test scan chains and test bus for correct function*
  - *Test digital hardware independently of analog/memory hardware using scan chains*
  - *Test memory hardware*
  - *Test analog hardware independently of other hardware using analog test bus*
  - *Test interconnections between digital/analog/memory hardware*

# IEEE 1149.4 Analog Test Bus

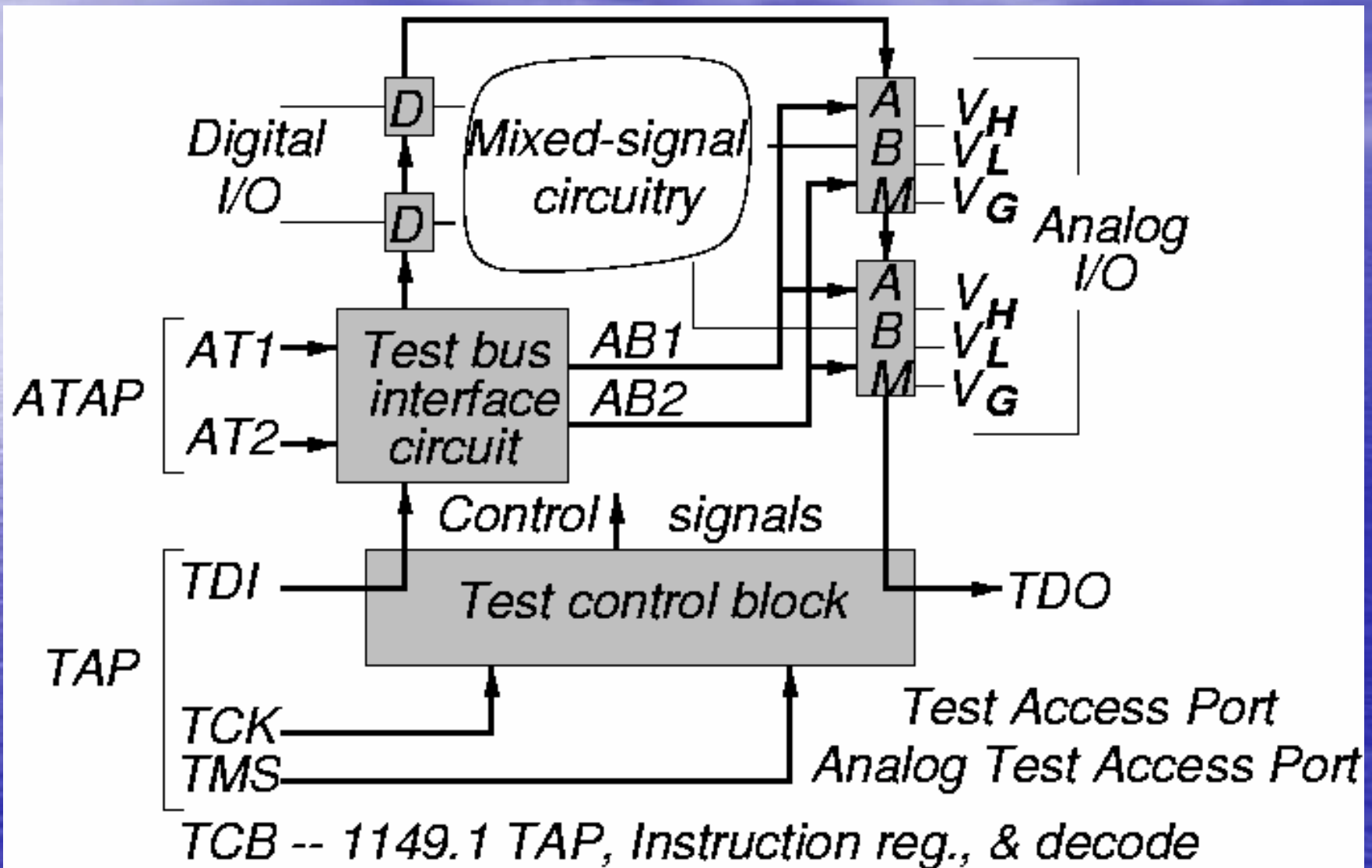


# *IEEE1149. 4 Analog Test Bus*

- 1149.4 analog test bus standard
  - *JTAG (IEEE 1149.1) with “Analog Test Bus”*
  - *Provides controllability and observability to all the analog blocks*
  - *Eliminates analog test points -- Decreases chip area*
    - Still excessive for scan chains/test bus
  - *Disadvantages*
    - Bus has less than 1 MHz bandwidth -- Unsuitable for testing high-frequency communications circuits
    - Bus may have 5% measurement error
    - Cannot move data very far on the bus
    - Systems with small amplitudes or high precision components cannot be tested
    - *No theory for testing combined analog/digital chip*




# Analog Boundary Module

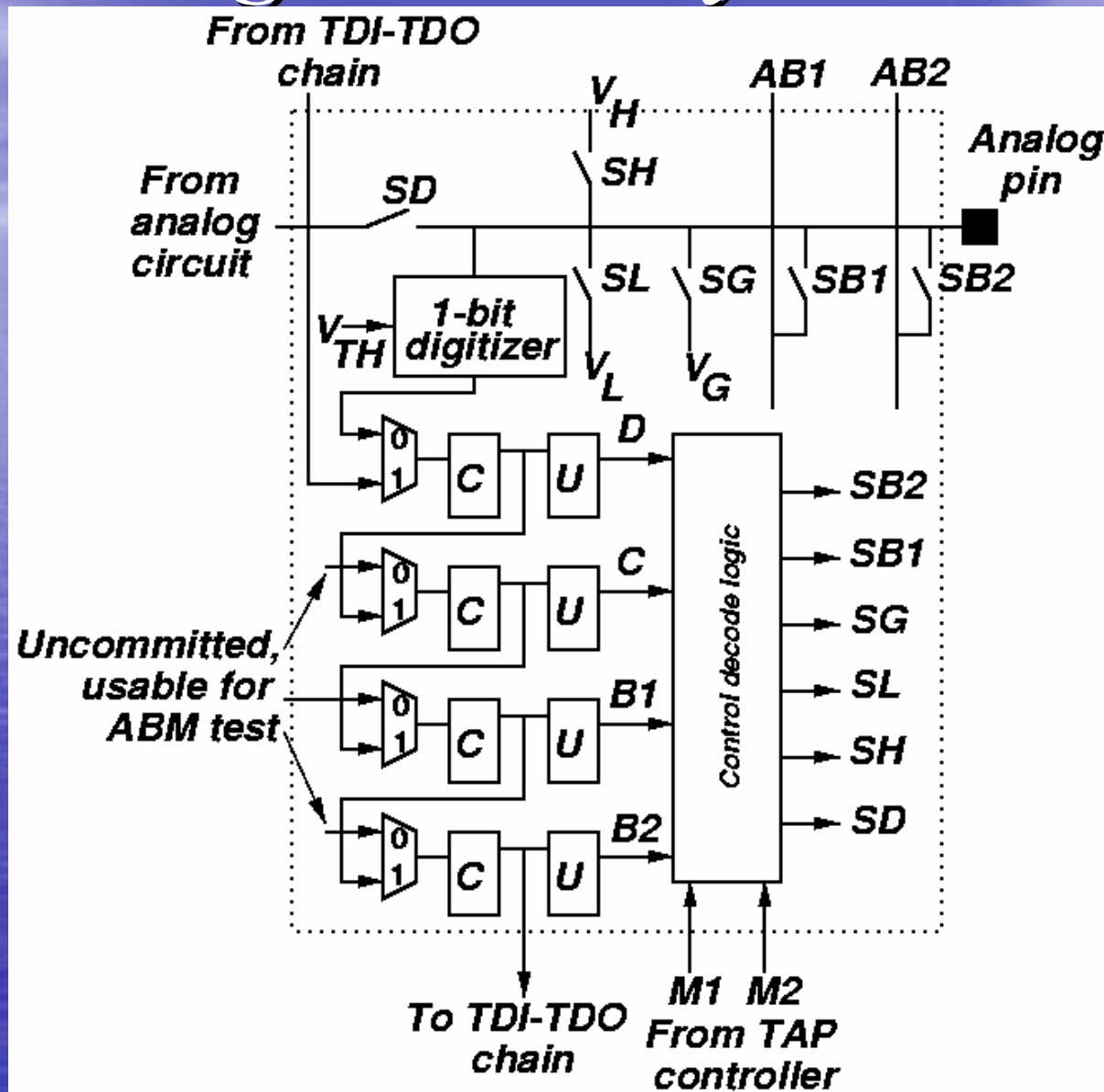

# *DSP Tester Concept for Mixed-Signal Circuits*

© 1987 IEEE

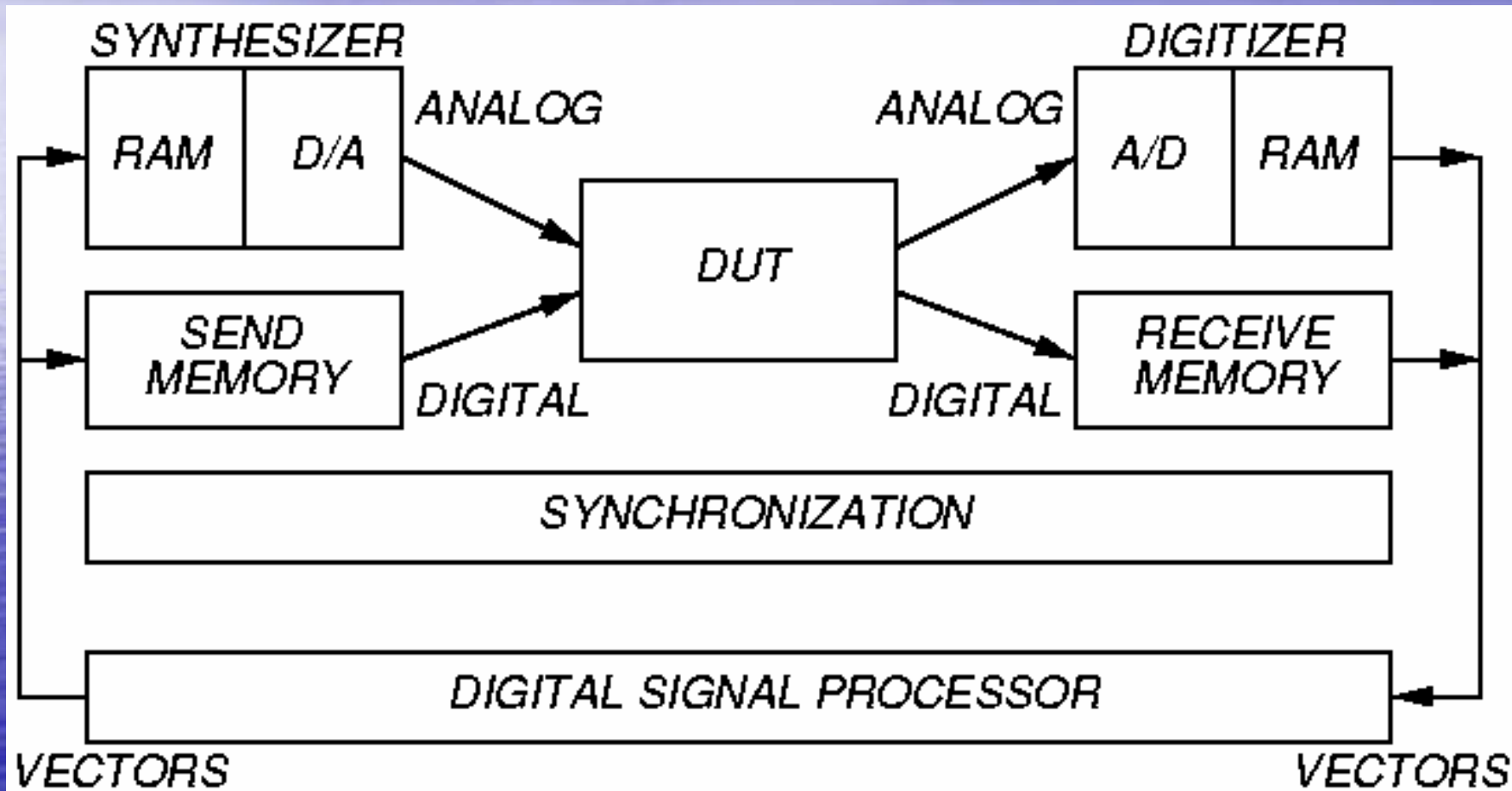

# *Prior Work – Analog Test*

- Slamani & Kaminska – Analog fault observability
- Hamida & Kaminska – Sensitivity analysis test generator
- Nagi *et al.* – *DRAFTS* – Analog fault simulator with SFGs
- Ramadoss & Bushnell – Signal flow graph test generator
- Roberts – MADBIST – Digital gen. of analog test wave
- Evans – Time domain analysis test generation
- Variyan and Chatterjee – Time domain sensitivity test generation for linear analog circuits
- Chakrabati & Chatterjee – Fault-oriented test gen.
- Su *et al.* – On-chip analog test waveform generation
- Lu *et al.* – Digital circuit for off-chip sine wave generator ( $\Sigma$ - $\Delta$ )
- Lu & Roberts – Multi-tone off-chip sine wave generator ( $\Sigma$ - $\Delta$ )

# *Correlation-Based Testing Using Transients*

*Evans, Al-Qutayri, and Shepherd*

*School of Electronic and Electrical Eng., U. of Bath*

- **New method to test mixed-signal ICs**
  - ***Test analog and digital parts together***
  - ***Used pulsed excitation of analog part***
  - ***Analyze transient response of digital outputs using a correlator***
    - **Composite transfer function and impulse response**
    - **Get test vectors from digital automatic test-pattern generation system**

# *Mathematical Analysis*


- Transient stimulus vector in mixed-signal circuit is digital test vector convolved with  $h(t)$  impulse of each propagating circuit block

$$Y(t) = [ x(t) * h(t) * z(t) ]$$

	<b>Analog</b>	<b>Digital</b>
<b>vector</b>	<b>Impulse</b>	<b>Impulse</b>
	<b>Response</b>	<b>Response</b>

- Correlate transient output signal  $y(t)$  with correlation signal  $p(t)$  derived from test vectors ( $x_n(t)$ )

# *Method Example*

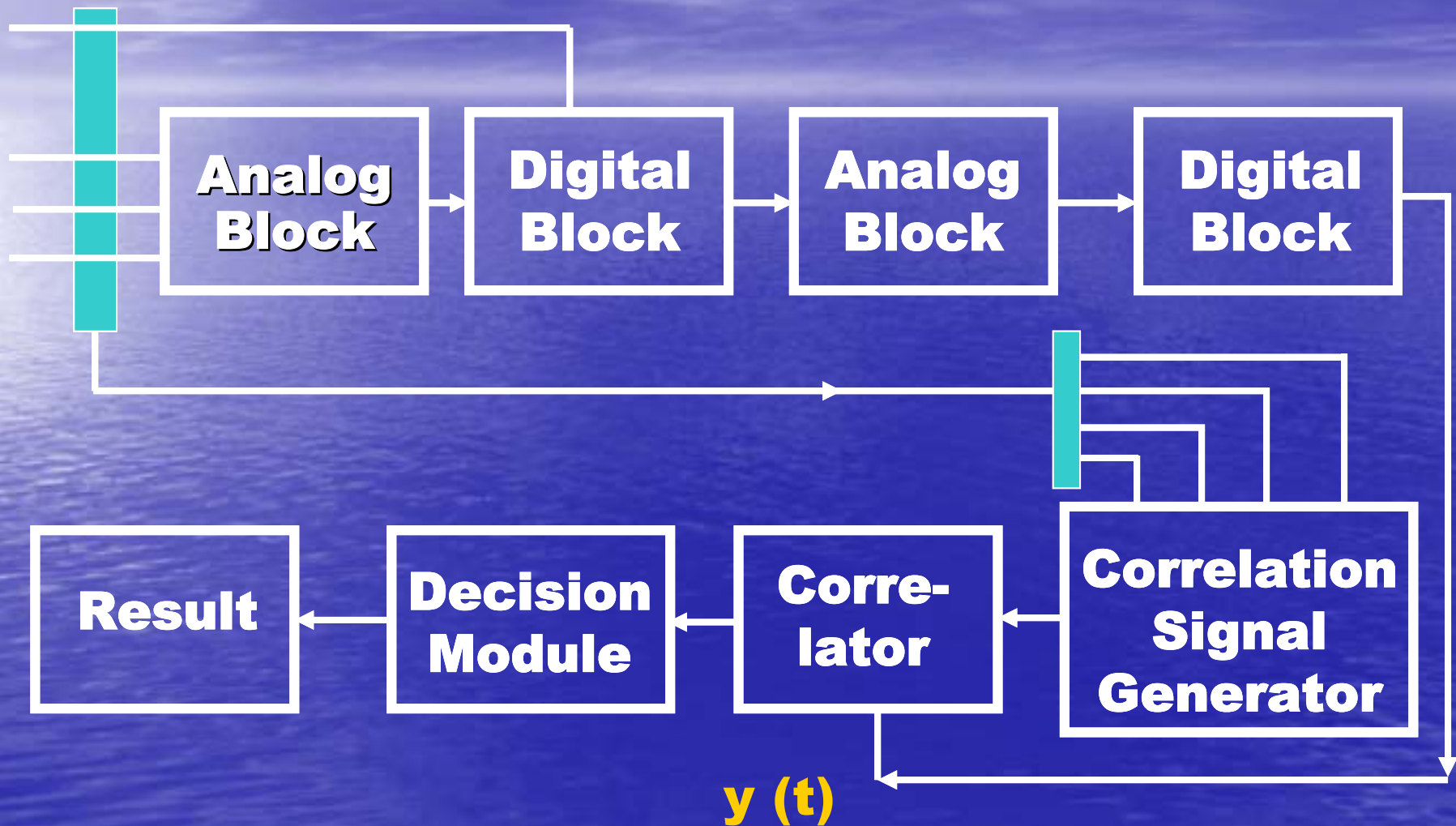

# *Correlation Analysis*

- Transient  $y(t)$  has 3 Fourier components:
  - *Fault condition components*
  - *Good machine components*
  - *Noise*

$$Y(j\omega) = [ \underset{\text{fault}}{Y_f(j\omega)} + \underset{\text{fault-free}}{Y_r(j\omega)} + \underset{\text{noise}}{Y_n(j\omega)} ]$$

- Get a correlation function  $R(y, p) =$  composite impulse response of IC signal path propagating circuit stimulus

# *Results*


- Tested OPAMP followed by digital circuit
- Modeled catastrophic analog faults (shorted and open components)
- Response was compared with fault dictionary to verify device
- 53 % fault coverage – some success, but unclear how well the method discriminates faults
- Short time stimulus is cause of low fault coverage




# *Digital Spectral Test Generation – Giani, Sheng, Hsiao, & Agrawal*

- Generate random vectors to test digital circuit
- Simulate good and faulty circuits with vector sequence – drop vectors that do not detect faults
- Calculate correlation of compacted vector sequence over time with spectral components
- Use Hadamard matrix and correlations to find digital spectrum of bit stream for an input
- Drop low correlation spectral components from test waveform sequence
  - *Equivalent to removing random noise from vector sequence*


# *Spectral Methods*

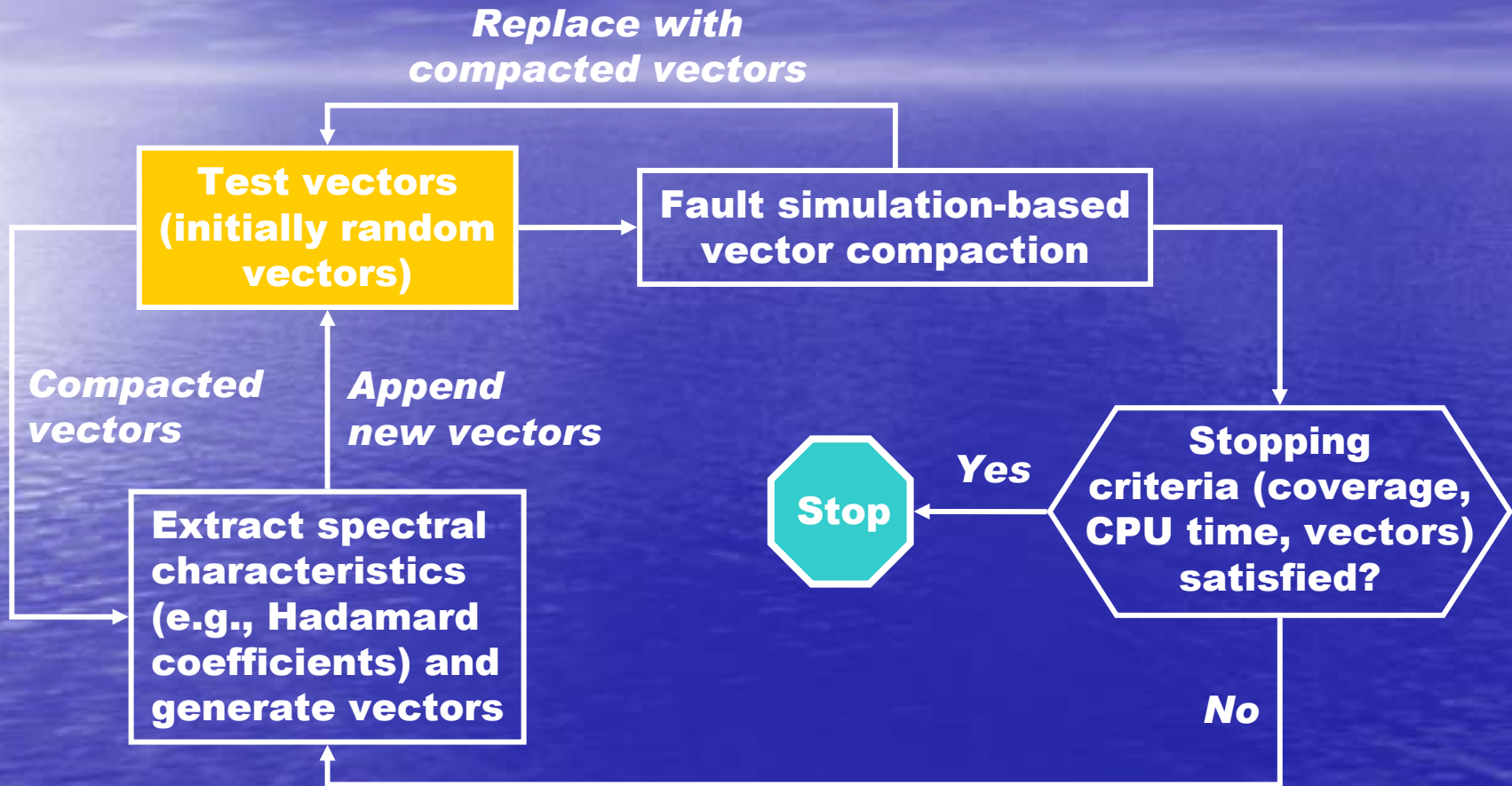
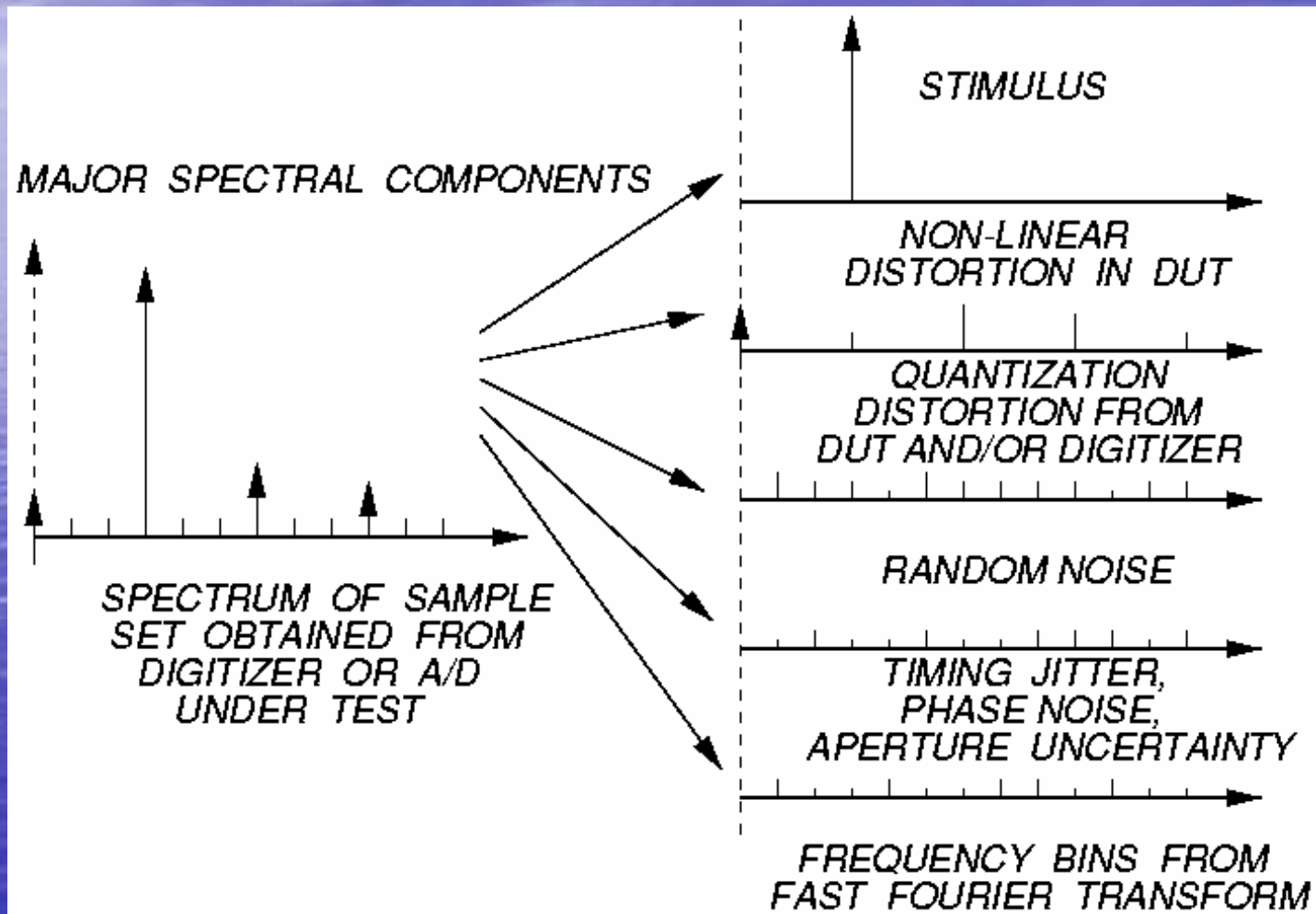
# *Spectral Components of Conventional Analog Test*


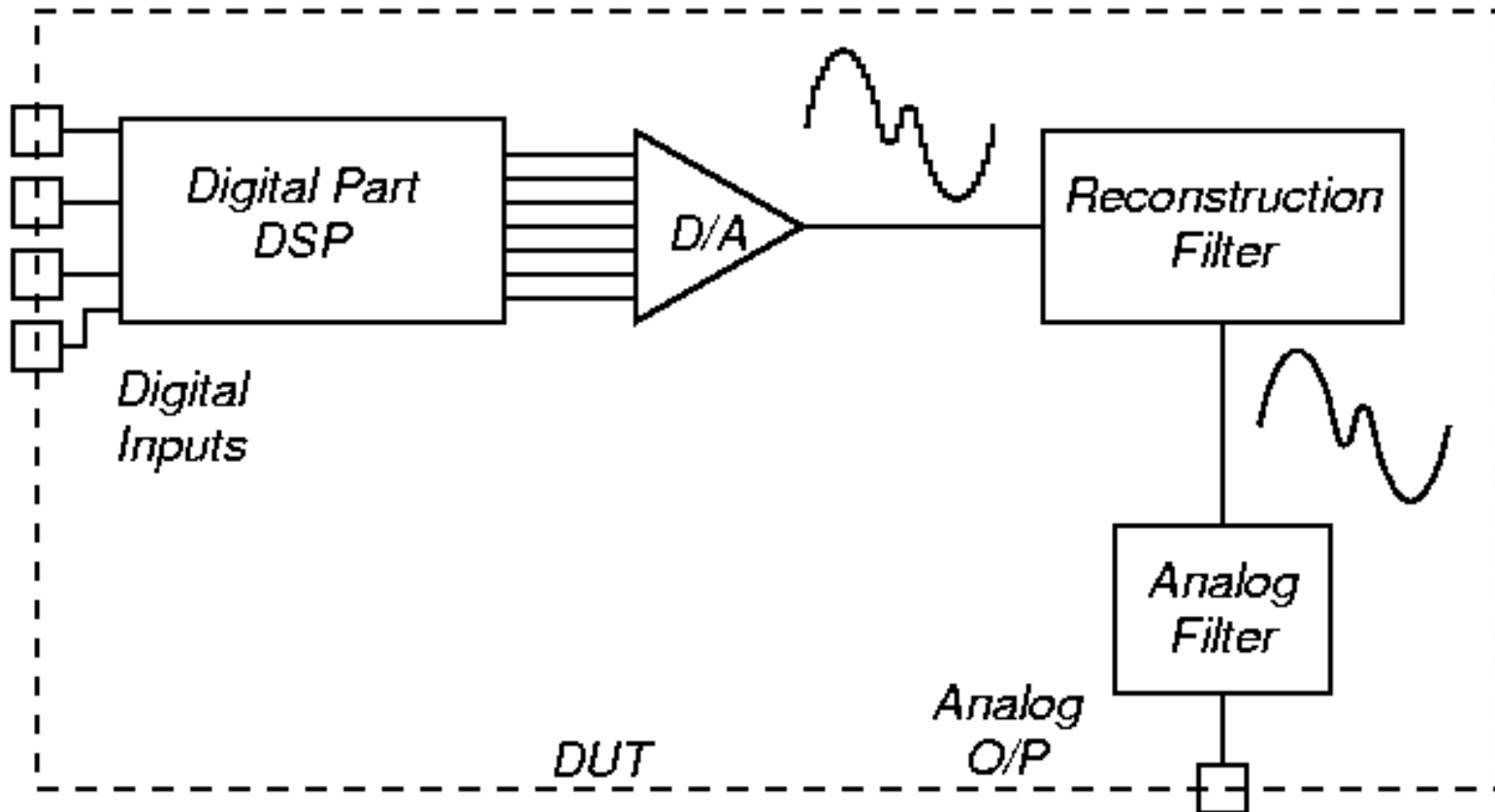
# *Proposed Combined Digital / Analog Test Method*



(a) Digital part used as pattern generator for analog part.

# *Proposed Method for Analog Module Testing*

- New automatic method to stimulate a digital circuit to produce analog tones needed for testing the analog part
  - *Frequently get tones near the frequency required to test analog circuit, but with additional spurious tones added*
- New automatic method to determine whether digitally-generated tones adequately test analog circuit for:
  - **Frequency response**
  - **Phase margin**
  - **Total Harmonic Distortion**
  - **Inter-modulation Distortion**

# *Test Frequency Generation with Combinational Circuits*

- Obtain digital test vector set (**in\_vector**) and output response set (**out\_vector**) (generate random vectors);
- Calculate cross-correlation of all input PIs (i) with each output PO j (**Cij**);
- Obtain the digitized version of the desired analog test waveform (**needed\_vectors**);
- For all vectors in **needed\_vector** (index i)
  - If some out\_vector matches needed\_vector [i]*  
**generated\_vector [i] = corresponding in\_vector;**
  - Else*  
Guess\_input\_stimuli () for the **needed\_vector [i]** ;  
Logic simulate the **guessed\_vectors** giving output **new\_vectors'** ;  
If some new\_vector' matches **needed\_vector [i]** use corresponding **guessed\_vector** ;  
Else use **guessed\_vector** giving closest matching **new\_vector'** ;

# *Guessing of Input Stimuli*


- $\text{Poll} = C \times \text{needed\_vector} / \# \text{POs}$ ;
- For all input correlations ( $\text{Poll}$ ) (index  $i$ )
  - If  $\text{Poll}[i] \geq 0.5$* 
    - Set bit  $i$  to 1 in all **guessed\_vectors**;
  - Else if  $\text{Poll}[i] \leq -0.5$* 
    - Set bit  $i$  to 0 in all **guessed\_vectors**;
  - Else if  $\text{Poll}[i] > 0$  and  $\text{Poll}[i] < 0.5$* 
    - Enumerate or randomly generate (with cellular automaton) vectors for bit  $i$  favoring 1;
  - Else if  $\text{Poll}[i] < 0$  and  $\text{Poll}[i] > -0.5$* 
    - Enumerate or randomly generate (with cellular automaton) vectors for bit  $i$  favoring 0;

# *Results for Single-tone Test with a Few Bits Directly Controlled*

CIRCUIT	# OF OUTPUT BITS	# OF BITS CONTROLLED	AVERAGE ERROR %	% HARDWARE SAVED
Adder8bit	9	1	0.00	88.88
Alu16bit	17	3	2.20	82.35
C432	7	2	0.08	71.43
C1908	25	2	0.64	92.00
C1355	32	2	1.24	93.75



 
# *Generated Waveforms with Combinational Circuits*



Sample Points

Generated Waveform with c1908

 


Sample Points

Generated Waveform with ALU, with 3  
bits directly controlled

# *Results for Multi-tone Test with a Few Bits Directly Controlled*

CIRCUIT	# OF OUTPUT BITS	# OF BITS CONTROLLED	AVERAGE ERROR %	% HARDWARE SAVED
Adder8bit	9	1	0.00	88.88
Alu16bit	17	3	1.67	82.35
C432	7	2	0.00	71.43
C1908	25	2	0.11	92.00
C1355	32	2	1.31	87.50


# *Required Multi-tone Waveform*

 

Sample Points

Required Multi-tone Waveform


3 tones: 2K, 3K, 7K Hz

 

Frequency in Hertz X 10<sup>4</sup>


Frequency Power Spectrum of the  
required Waveform
 
# *Generated Waveforms with Combinational Circuits*



Sample Points

Generated waveform with C1908

 

Frequency in Hertz X  $10^4$

Frequency power spectrum of the  
waveform

# *Test Frequency Generation with Sequential Circuits*

- Difficulties with sequential circuits
  - *Output does not depend only on the input values*
  - *For the same input vector output may be different depending upon the current state of the circuit*
  - *Generating a set of vectors strictly in a desired order not trivial*
- Our approach
  - *Consider PPI (Pseudo Primary Input) and PPO (Pseudo Primary Output) values in every clock cycle*
  - *Does not assume any scan hardware for the flip-flops*


# *Pseudo Primary Inputs (PPI) and Pseudo Primary Outputs (PPO)*

- Pseudo Primary Inputs (PPI) and Pseudo Primary Outputs (PPO)
  - *For a single clock cycle*
    - Flip-flop outputs can be modeled as PPIs
    - Flip-flop inputs can be modeled as PPOs
  - *PPO values for one clock cycle will be the PPI values for next cycle*
  - *PPO values are also stored during the logic simulation step along with PO values*
  - *While simulating the circuit with **guessed vectors**, PPO value corresponding to last vector is used as the PPI value*

# *Results for Single-tone Test with a Few Bits Directly Controlled*


CIRCUIT	# OF OUTPUT BITS	# OF BITS CONTROLLED	AVERAGE ERROR %	% HARDWARE SAVED
Piir8o	8	2	1.88	75.00
Pcont2	8	2	1.67	75.00
S1488	19	5	11.63	73.67
S1196	14	5	4.34	64.28
S1238	14	4	2.74	71.42
Am2910	16	4	6.37	75.00
 
# *Generated Waveforms with Sequential Circuits*



Sample Points

**Generated Waveform with piir8o**

 


Sample Points

**Generated waveform with 2 bits  
directly controlled**



 
# *Generated Waveforms with Sequential Circuits*



Sample Points

**Generated Waveform with s1238**

 


Sample Points

**Generated waveform with 4 bits  
directly controlled**

# *Results for Multi-tone Test with a Few Bits Directly Controlled*

CIRCUIT	# OF OUTPUT BITS	# OF BITS CONTROLLED	AVERAGE ERROR %	% HARDWARE SAVED
Piir8o	8	2	0.84	75.00
Pcont2	8	2	0.36	75.00
S1488	19	5	6.41	73.67
S1196	14	4	2.86	71.42
S1238	14	3	1.39	78.57
Am2910	16	4	1.36	75.00

 
# *Generated Multi-tone Waveforms with Sequential Circuits*



Sample Points

Generated waveform with piir8o

With 2 bits directly controlled

 


Frequency in Hertz X  $10^4$

Frequency power spectrum of the  
waveform
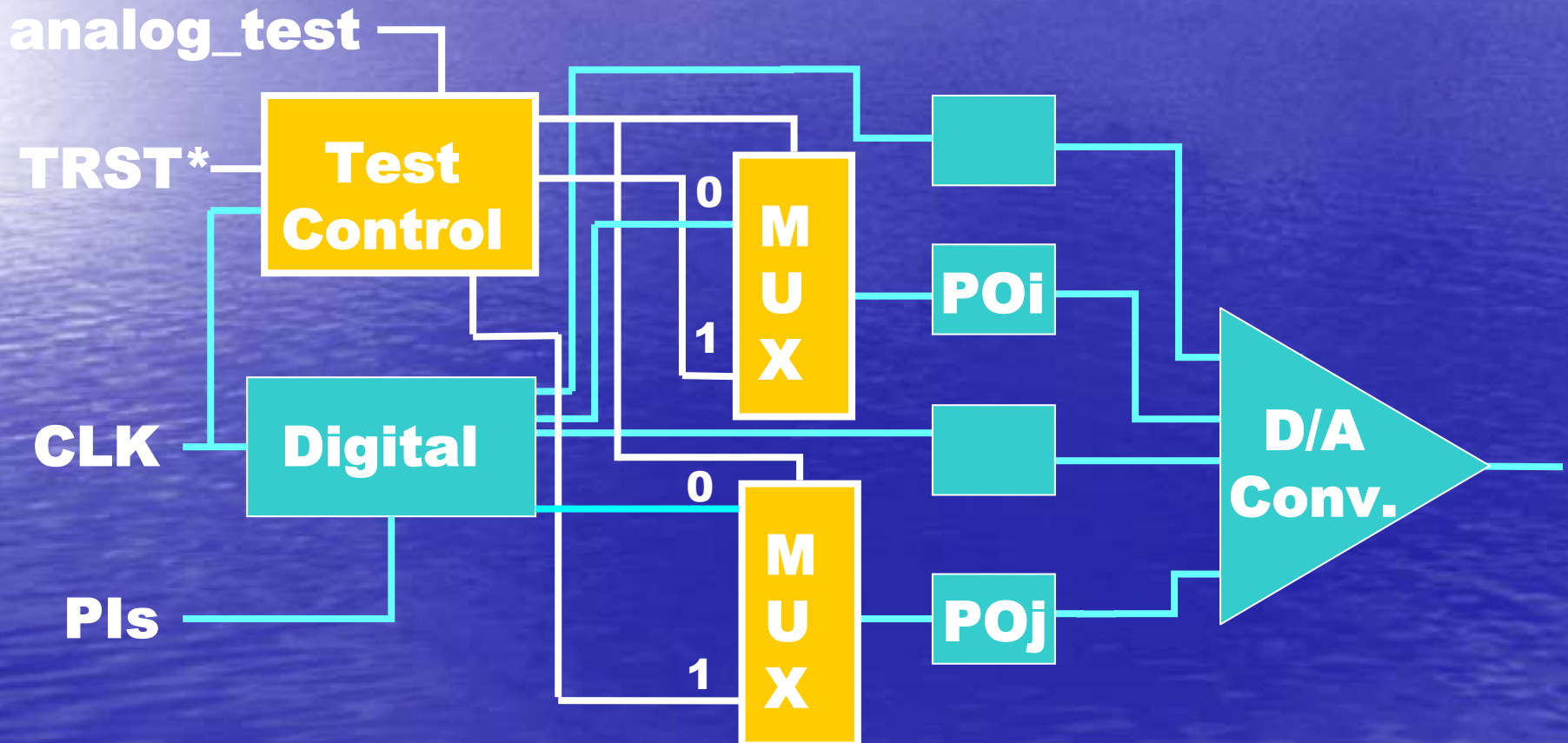
# *Example Bit Control Hardware*

- Add local controller that steps bits PO<sub>i</sub> to PO<sub>j</sub> through needed sequence for test waveform period
- Needs 1 PI – analog\_test and 1 MUX per controlled bit



# *Analysis of Digital Module Fault Detectability*

- Through analog output module
- Must account for analog circuit good machine noise
- $Y(j\omega) = X(j\omega) \times H(j\omega) + D(j\omega) \times H(j\omega) + N(j\omega)$

<b>Input</b>	<b>Analog</b>	<b>Error</b>	<b>Good</b>
<b>Analog</b>	<b>Trans.</b>	<b>Caused by</b>	<b>Analog</b>
<b>Signal</b>	<b>Funct.</b>	<b>Digital</b>	<b>Circuit</b>
		<b>Fault</b>	<b>Noise</b>

- Consider a digital fault detected if it causes a 10% magnitude or phase shift in Fast Fourier Transform of output analog signal

# *Results: With ATPG Vectors*

<b>Circuit</b>	<b>Total # of Faults</b>	<b>Faults Detected by power spectrum analysis</b>	<b>Faults Detected by phase spectrum analysis</b>	<b>% Fault Coverage</b>
<b>Adder8bit</b>	<b>128</b>	<b>94</b>	<b>34</b>	<b>100</b>
<b>ALU 16-bit</b>	<b>1808</b>	<b>740</b>	<b>1068</b>	<b>100</b>
<b>C432</b>	<b>519</b>	<b>496</b>	<b>23</b>	<b>100</b>
<b>C1355</b>	<b>1198</b>	<b>544</b>	<b>654</b>	<b>100</b>

# *Conclusions*

- Showed how to reconfigure common digital blocks that drive on-chip analog circuits as:
  - *Analog multi-tone waveform generator*
- Results show capability of generating internal analog multi-tone waveforms in a variety of circuits
  - *New DFT method for controlling very few digital O/P bits to improve analog test waveform quality*
  - *Very low chip area overhead*
  - *Eliminates analog test bus and on-chip analog waveform generator*
- 1st use of analog circuit spectral analysis for detecting internal digital sa0, sa1 faults